

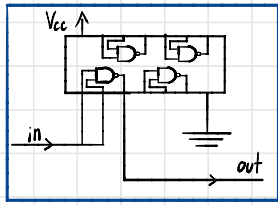


Oscillator Circuit

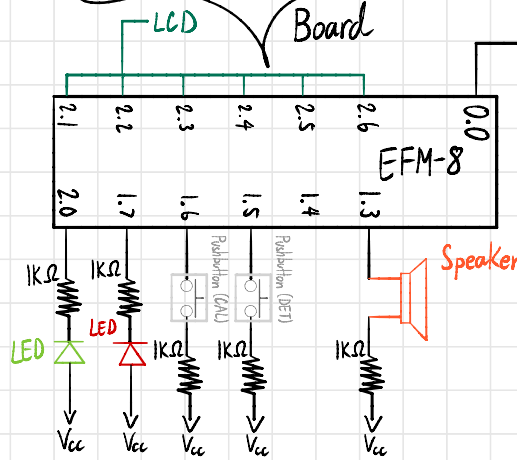

Using NAND gate
CD74HC00E

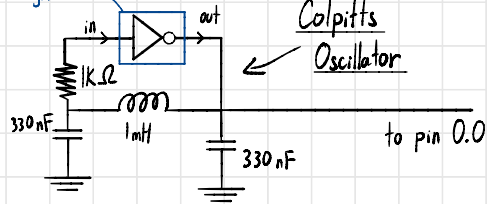

Board

Oscillator circuit